

Attempt in all questions and assume any missing data.

Q1:(a)-For the following measurements data sets:

Data Set A:	24.3643	21.1894	23.2292	24.8344	23.3247
	24.3519	20.0496	20.6850	24.0938	22.1508.
Data Set B:	23.7683	23.9694	24.5998	24.2236	21.8388
	23.1040	23.6564	20.9695	24.5241	22.8460.

Calculate **mean, median, standard deviation** and **the variance** for each of the data set shown above. Which one is accurate? **(8 Marks)**

(b)-Three resistances have the following ratings: $R_1 = 15 \Omega \pm 5 \%$; $R_2 = 33 \Omega \pm 2 \%$; $R_3 = 75 \Omega \pm 5 \%$. Determine the magnitude and limiting error in ohms, if the resistances are connected: 1-in **series**, 2-in **parallel**. Also obtain percentage relative limiting error in the resultant. **(8 Marks)**

Q2:(a)-A voltmeter having a sensitivity of $2 \text{ k}\Omega/\text{V}$ reads 90 V on its 150V range, when connected across an unknown resistor in series with an ammeter. The ammeter resistance is 100Ω and reads 30 mA . Calculate:

1-Apparent resistance. 2-Actual resistance of unknown resistor. 3-Error due to loading effect of voltmeter. 4-Percentage relative accuracy. **(8 Marks)**

(b)-**Figure (1)** shows a simple series circuit of R_1 and R_2 connected to a 250 V DC source. If the voltage across R_2 is to be measured by the voltmeters having: 1-A sensitivity of $500 \Omega/\text{V}$, 2-A sensitivity of $10,000 \Omega/\text{V}$. Find which voltmeter will read more accurately. Both the meters are used on the 150 V range. **(8 Marks)**

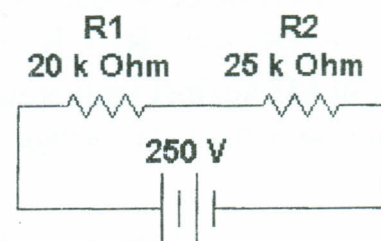


Figure (1)

Q3:(a)-A moving coil instrument gives a full scale deflection for a current of 20 mA with a potential difference of 200 mV across it. Calculate: 1-**Shunt resistor** required to use it as an ammeter to get a range of $0 - 200 \text{ A}$.

2-Multiplier required to use it as a voltmeter of range $0-500 \text{ V}$. **(8 Marks)**

(b)-A basic D'Arsonval movement with an internal resistance of 50Ω and a full scale deflection current of 2 mA is to be used as a multirange voltmeter. The voltage ranges are $0-10 \text{ V}$, $0-50\text{V}$, $0-100 \text{ V}$, $0-500 \text{ V}$. 1- Design the series string multipliers. 2- Design the individual multipliers. **(8 Marks)**

Q4:(a)-A D'Arsonval movement with an internal resistance of 730Ω and full scale current of 5mA is available. A multirange ammeter with the ranges of 1A , 5A , and 25A is employing: 1-Derive an expression for **individual** shunts and

calculate its values. (2)- Derive an expression for **Aryton** shunts and calculate its values. **(8 Marks)**

(b)-A 50Ω basic movement requiring a full scale current of 1 mA is to be used as an ohmmeter. The internal battery voltage is 3 V . A half scale deflection marking desired is $1 \text{ k}\Omega$. Calculate: 1-Values of R_1 , and R_2 . 2-Maximum value of R_2 to compensate for a 5% drop in battery voltage. **(8 Marks)**

Q5:(a)-The four arms of the Wheatstone bridge, shown in **Figure (2)**, have the following resistances; $AB = 1 \text{ k}\Omega$, $BC = 1 \text{ k}\Omega$, $CD = 120 \Omega$, and $DA = 120 \Omega$. The bridge is used for strain measurement and supplies from 5 V ideal battery. The galvanometer has sensitivity of $1 \text{ mm}/\mu\text{A}$ with internal resistance of 200Ω . Determine the deflection of the galvanometer if arm DA increases to 121Ω and arm CD decrease to 119Ω . **(9 Marks)**

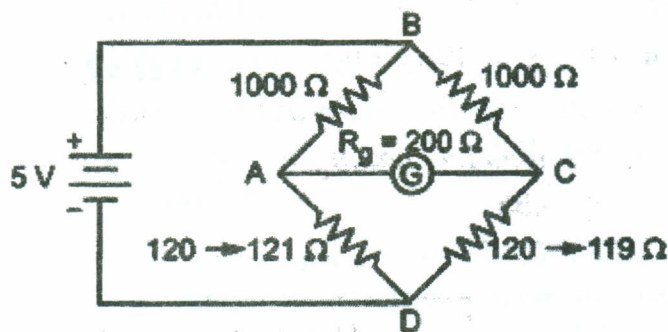


Figure (2)

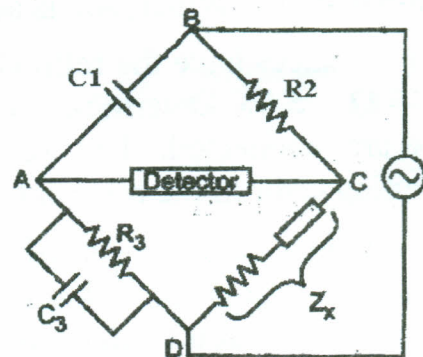


Figure (3)

(b)-The temperature dependent resistor is used in one arm of a Wheatstone bridge. The other resistances $R_1 = R_2 = R_3 = 6 \text{ k}\Omega$ and $V = 10 \text{ V}$. The variation of resistance in $\text{k}\Omega$ against temperature is given by: $R = 2 + t/20 \text{ k}\Omega$. Calculate the temperature at which the bridge is balanced. Also calculate the error voltage at 55°C and 95°C . **(9 Marks)**

Q6:(a)-The AC bridge shown in **Figure (3)** is balanced at 1 kHz . It has following components: $C_1 = 0.2 \mu\text{F}$, $R_2 = 500 \Omega$, $R_3 = 300 \Omega$, and $C_3 = 0.1 \mu\text{F}$. Derive an expression for the unknown impedance Find the value of Z_x . **(9 Marks)**

(b)-For the **Wien** bridge shown in **Figure (4)**, derive an expression for the frequency f of this bridge at a balance condition. Also find the equivalent parallel resistance and capacitance that causes a **Wien** bridge to null with the following component values: $R_1 = 2.7 \text{ k}\Omega$, $C_1 = 5 \mu\text{F}$, $R_2 = 22 \text{ k}\Omega$, $R_4 = 100 \text{ k}\Omega$. The operating frequency is 2.2 kHz .

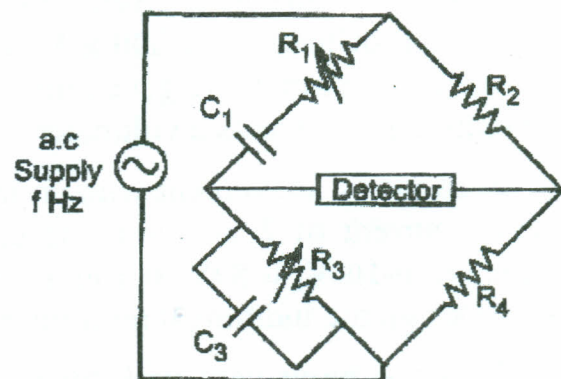


Figure (4)

(9 Marks)